


BJT AMPLIFIERS

1. Two-port system
2. BJT configurations
3. Voltage Buffer
4. Current Buffer

BJT AMPLIFIERS

1. Two-port system
2. BJT configurations
3. Voltage Buffer
4. Current Buffer




two port system

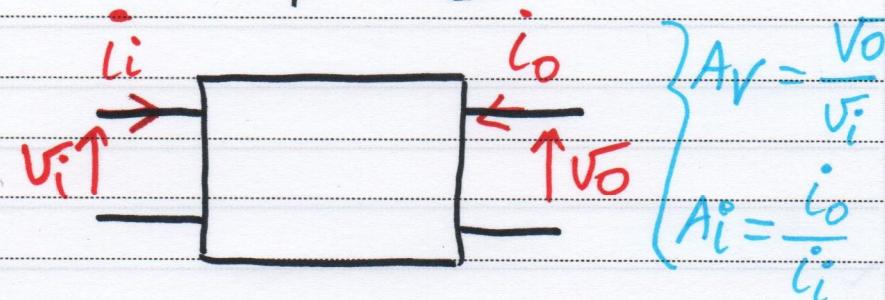


$$\left. \begin{array}{l} A_v = \frac{v_o}{v_i} \\ A_{i_o} = \frac{i_o}{i_i} \end{array} \right\}$$

BJT AMPLIFIERS

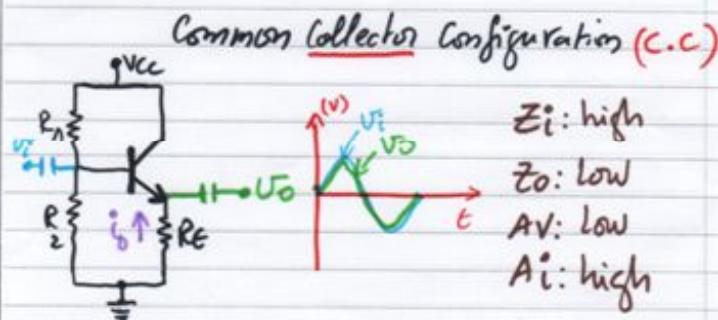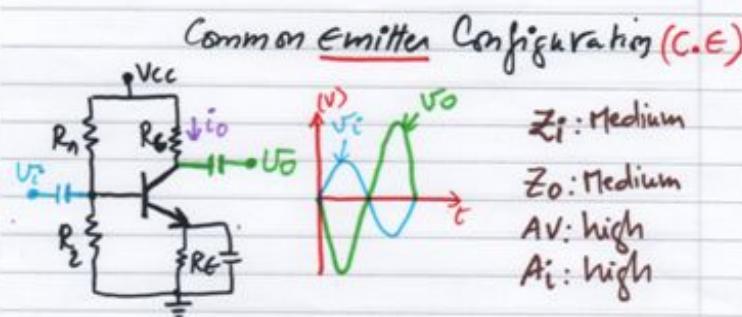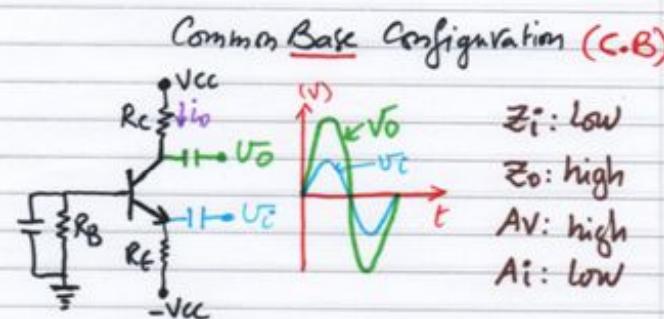1. Two-port system
2. BJT configurations
3. Voltage Buffer
4. Current Buffer




BJT Amplifier using voltage dep. source

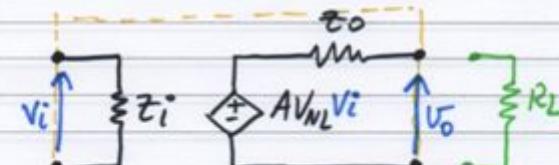

A_{VNL} : is The No loaded gain in Voltage.

BJT Amplifier using current dep. source

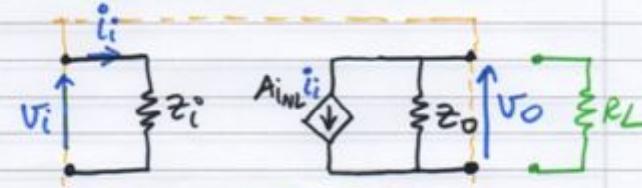


A_{iNL} : is The No loaded gain in current.

In The Case of (common base Config)


$$A_{iNL} \approx -1$$

BJT AMPLIFIERS

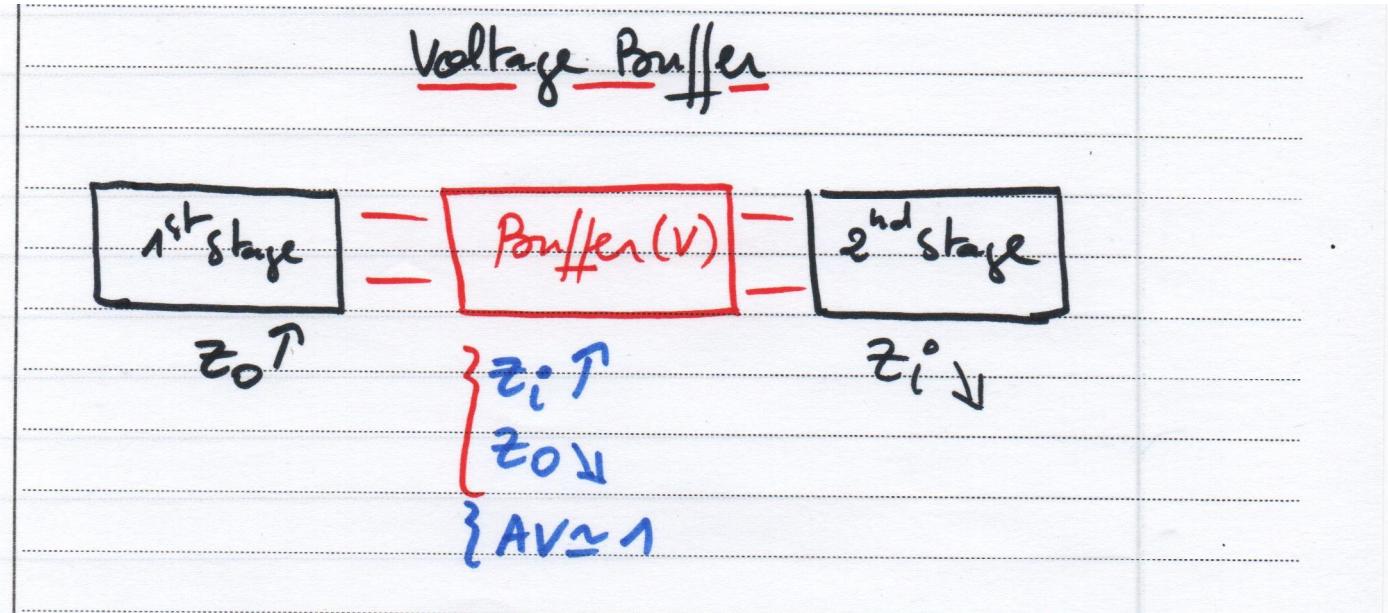
1. Two-port system
2. BJT configurations
3. **Voltage Buffer**
4. Current Buffer



Application:

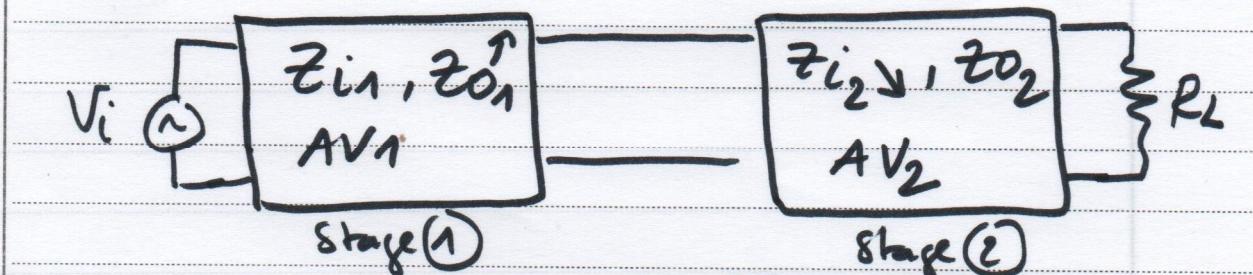

$$\underline{AV_L ??}$$

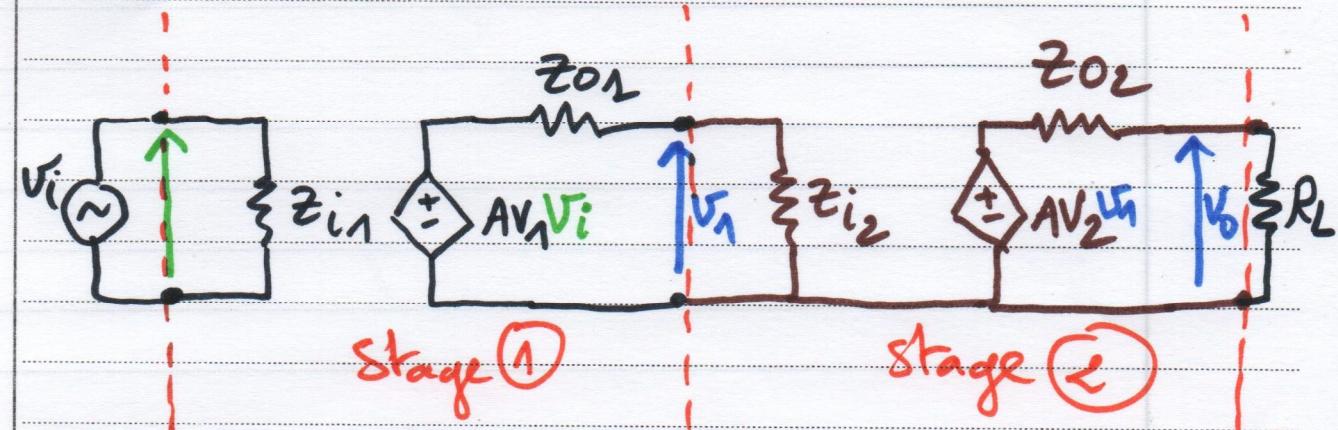

$$V_1 = \frac{z_{i2}}{z_{i2} + z_{o1}} AV_1 V_i \dots \textcircled{1}$$

$$V_0 = \frac{R_L}{R_L + z_{o2}} AV_2 V_1 \dots \textcircled{2}$$

\textcircled{1} in \textcircled{2}:

$$V_0 = \frac{R_L}{R_L + z_{o2}} \times \frac{z_{i2}}{z_{i2} + z_{o1}} AV_1 AV_2 V_i$$

$$AV_L = \frac{V_0}{V_i} = \frac{R_L}{R_L + z_{o2}} \times \frac{z_{i2}}{z_{i2} + z_{o1}} + AV_1 \times AV_2$$

If we suppose: $z_{O_2} = M$, $R_L = M$
with: $z_{O_2} = H$, $z_{i_2} = L$



$$AV_L = \frac{R_L \xrightarrow{M}}{R_L + z_{O_2}} \times \frac{z_{i_2} \xrightarrow{L}}{z_{i_2} + z_{O_2}} \times AV_1 \times AV_2$$

$\underbrace{\qquad\qquad}_{\approx 1/2}$ $\underbrace{\qquad\qquad}_{\approx 0}$


!!!

$$\boxed{AV_L \approx 0}$$

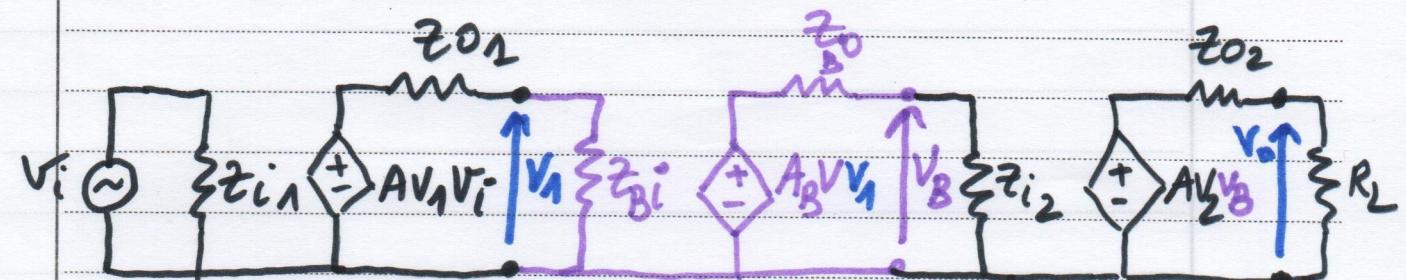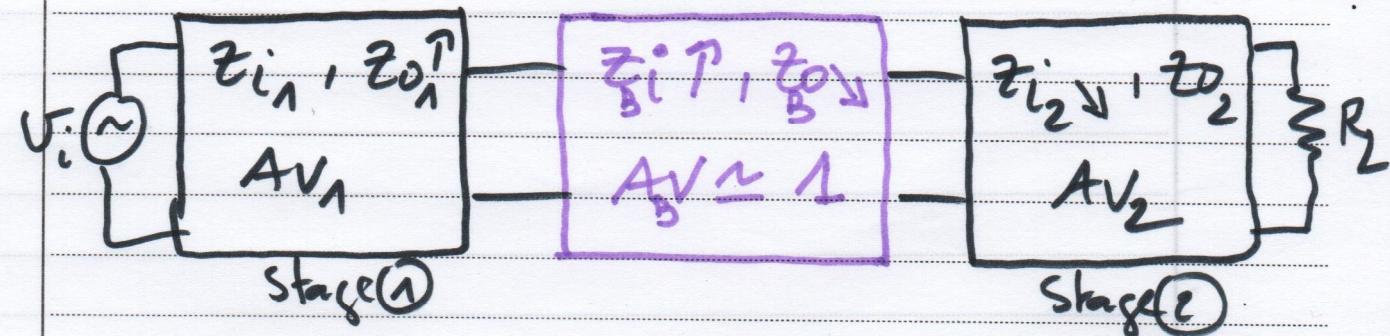Solution \Rightarrow Adding a Voltage Buffer



The new AV_L ??

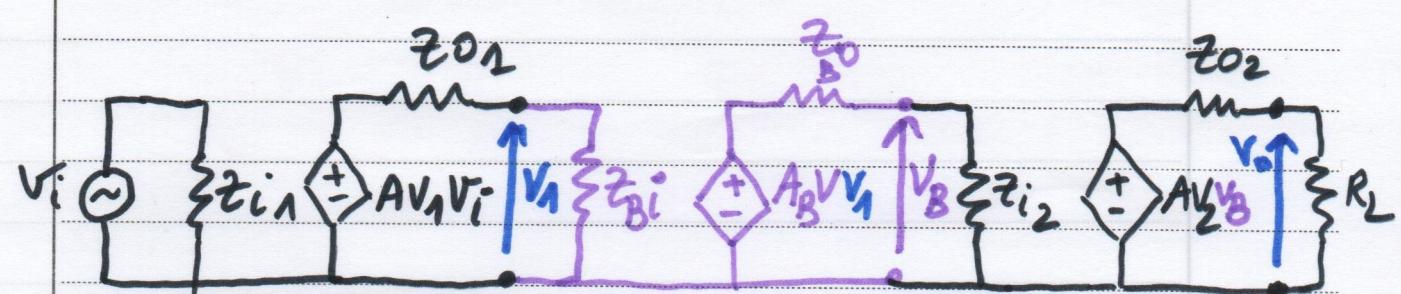

The new AV_L ??

$$V_o = \frac{R_L}{Z_{O2} + R_L} A V_2 V_B \dots \textcircled{1}$$

$$V_B = \frac{Z_{i2}}{Z_{i2} + Z_{B2}} A_B V_1 \dots \textcircled{2}$$

$$V_1 = \frac{Z_{Bi}}{Z_{Bi} + Z_{O1}} A V_i V_i \dots \textcircled{3}$$

③ in ② and ② in ① \Rightarrow


$$AV_L = \frac{V_o}{V_i} = \frac{R_L \cancel{M}}{\cancel{Z_{O_2}} + R_L} \times \frac{\cancel{Z_{i_2}} \cancel{L}}{\cancel{Z_{i_2}} + \cancel{Z_{BQ}}} \times \frac{\cancel{Z_{B_i}} \cancel{H}}{\cancel{Z_{B_i}} + \cancel{Z_{D_1}}} AV_1 \times AV_2 \times ABV$$

\cancel{M} \cancel{L} \cancel{H}
 \cancel{M} \cancel{L} \cancel{L}
 \cancel{H} \cancel{H}

$\approx 1/2$ $\approx 1/2$ $\approx 1/2$

$$AV_L \neq 0$$

Example:

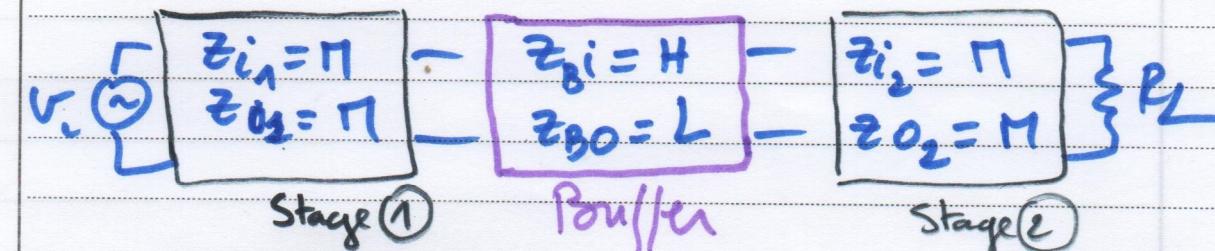

$$AV_L = \frac{V_o}{V_i} = \frac{R_L}{z_{o_2} + R_L} \times \frac{z_{i_2}}{z_{i_2} + z_{b_0}} \times \frac{z_{b_i}}{z_{b_i} + z_{o_1}}$$

Annotations: $\frac{R_L}{z_{o_2} + R_L} \approx 1$, $\frac{z_{i_2}}{z_{i_2} + z_{b_0}} \approx 1$, $\frac{z_{b_i}}{z_{b_i} + z_{o_1}} \approx 1$


$AV_1 AV_2 AB_V$
 $" " 1$

AV_L (without buffer) ≈ 0


$$AV_L \text{ (with buffer)} \approx \frac{R_L}{z_{o_2} + R_L} AV_1 \times AV_2$$

BJT AMPLIFIERS

1. Two-port system
2. BJT configurations
3. Voltage Buffer
4. Current Buffer

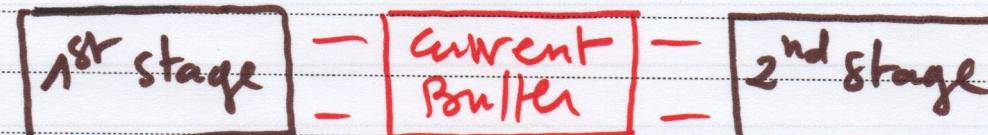
Current Buffer

$$\left. \begin{array}{l} z_i \downarrow \\ z_0 \uparrow \\ A_i \approx 1 \end{array} \right\}$$

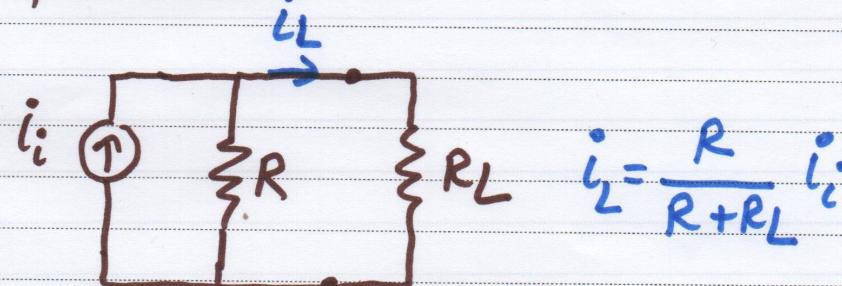Application


If $RL \uparrow$ and $R \downarrow \Rightarrow i_L \approx 0$

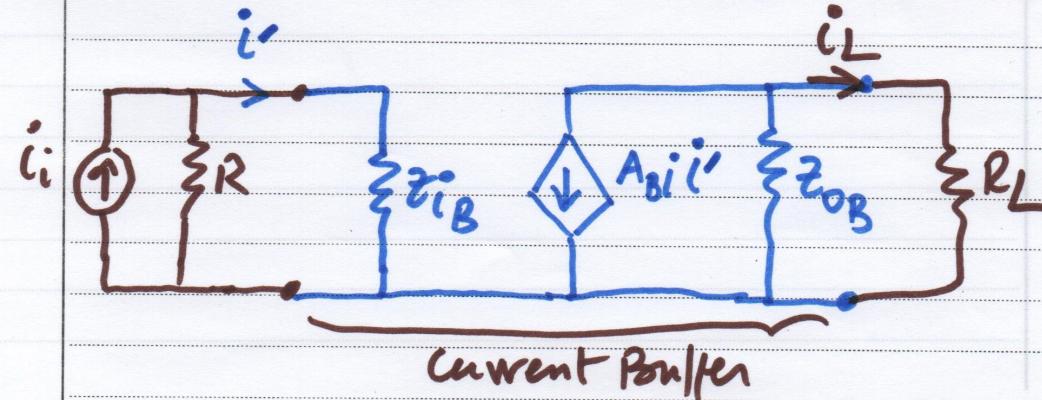To increase The level of The output Current
 \Rightarrow We Have to add a Current Buffer



Current Buffer \Rightarrow Common base configuration

z_{iY} , z_{oP} and $A_i \approx -1$

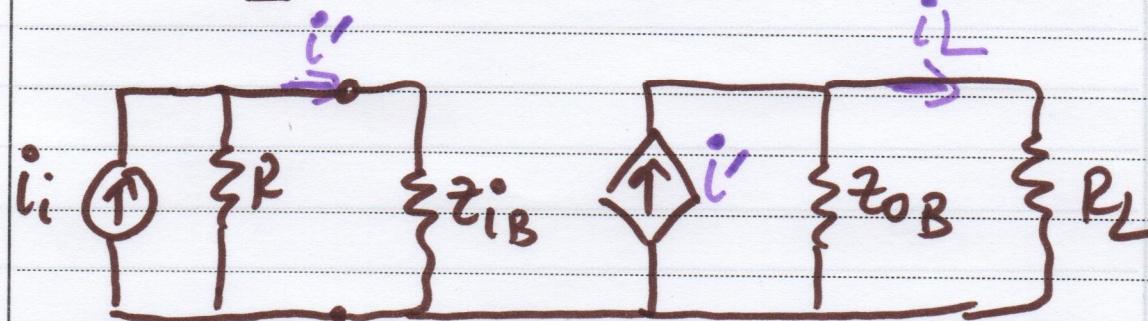

$$i_L = \frac{z_{oB}}{z_{oB} + R_L} i' \dots \textcircled{1}$$

$$i' = \frac{R}{R + z_{iB}} i_i \dots \textcircled{2}$$

② in ①

$$i_L = \frac{Z_{OB}^H}{Z_{OB} + R_L} \times \frac{R^L}{R + Z_{OB}} i_i$$

$H \downarrow \quad H \downarrow \quad L \downarrow \quad L \downarrow$

$\overbrace{Z_{OB}}^{1/2} \quad \overbrace{R_L}^{1/2}$

The best Case: $R=1$ and $R_L=1$

$$i_L \approx i_i$$