
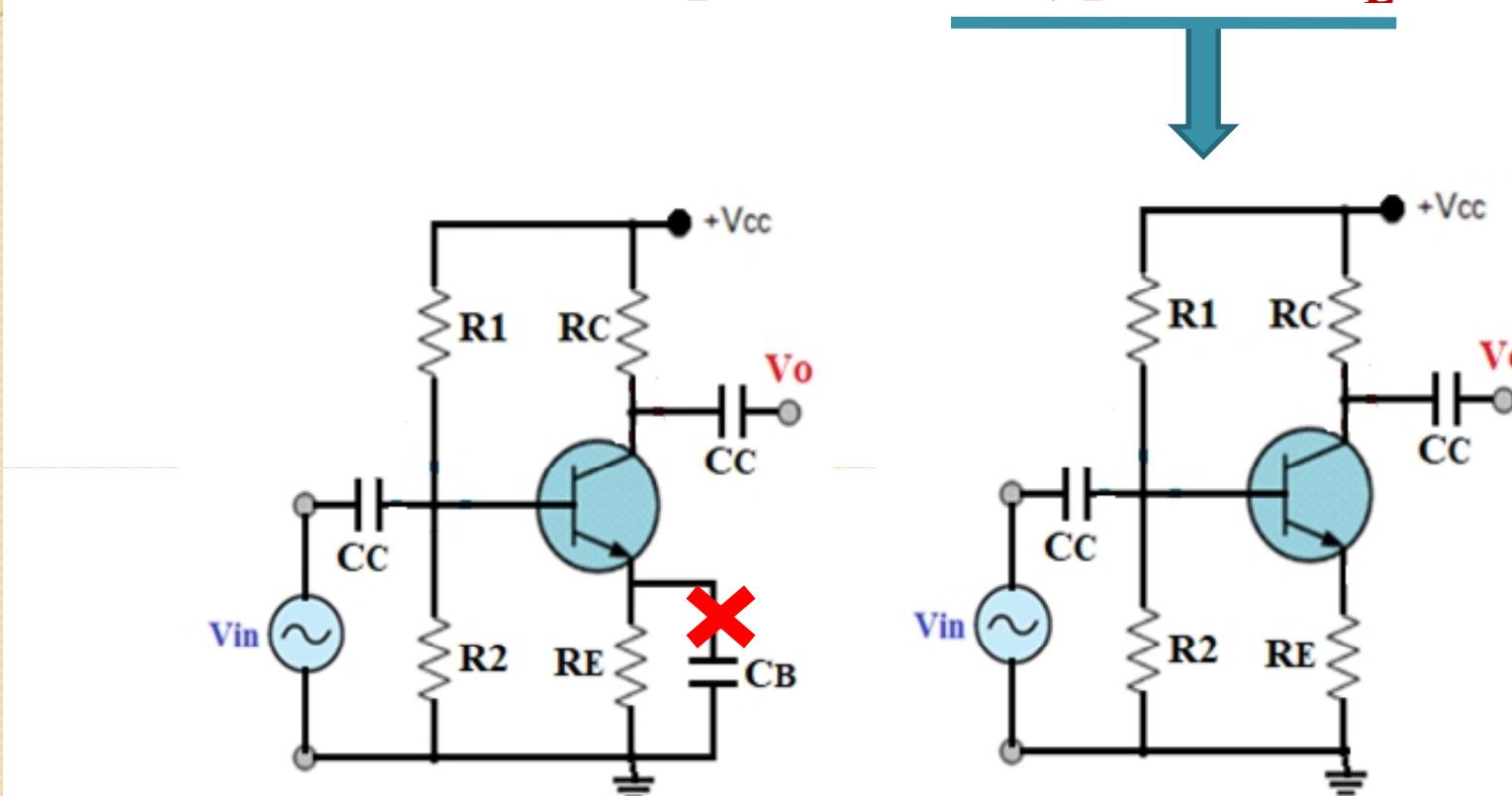




App 2: Common Emitter Voltage divider bias amplifier (unbypassed R_E)

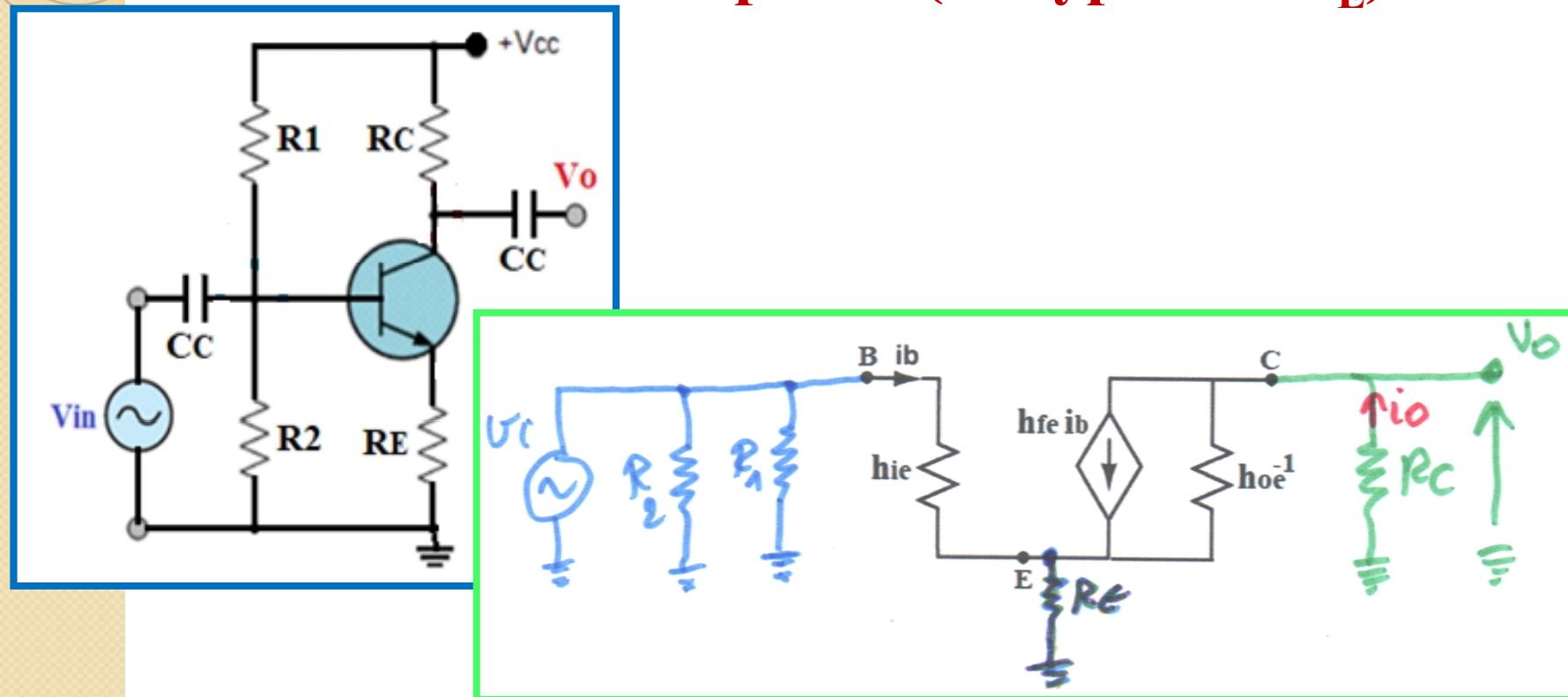



App 2: Common Emitter Voltage divider bias amplifier (unbypassed R_E)




App 2: Common Emitter Voltage divider bias amplifier (unbypassed R_E)

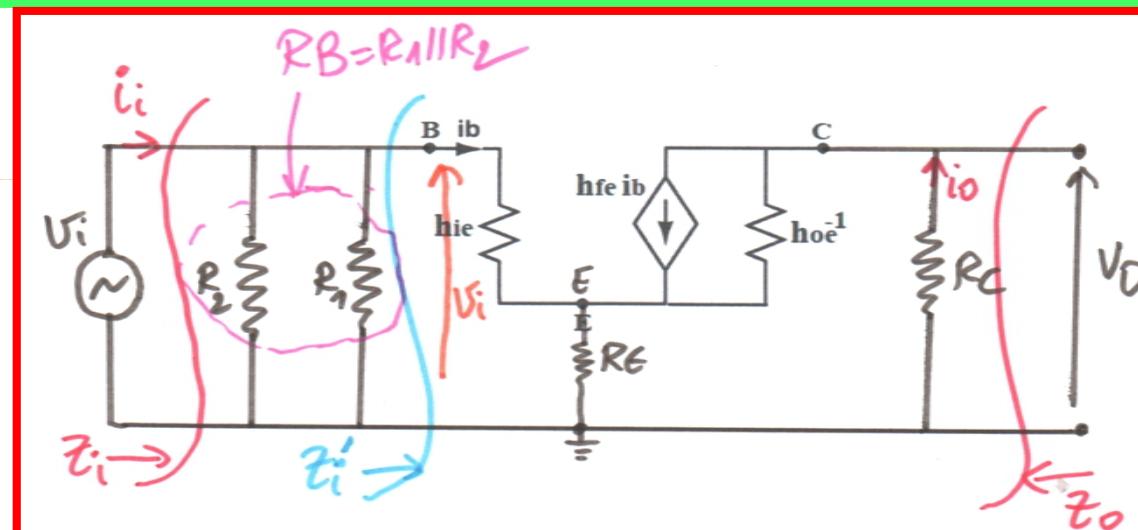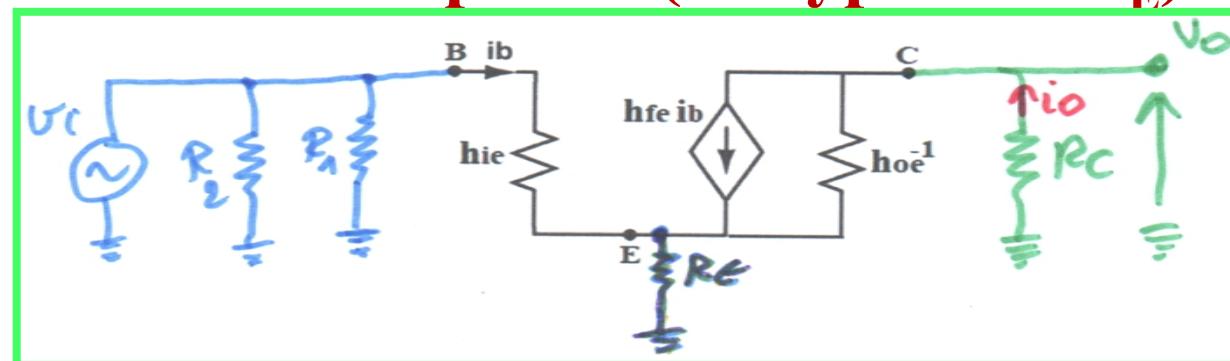

App 2: Common Emitter Voltage divider bias amplifier (unbypassed R_E)

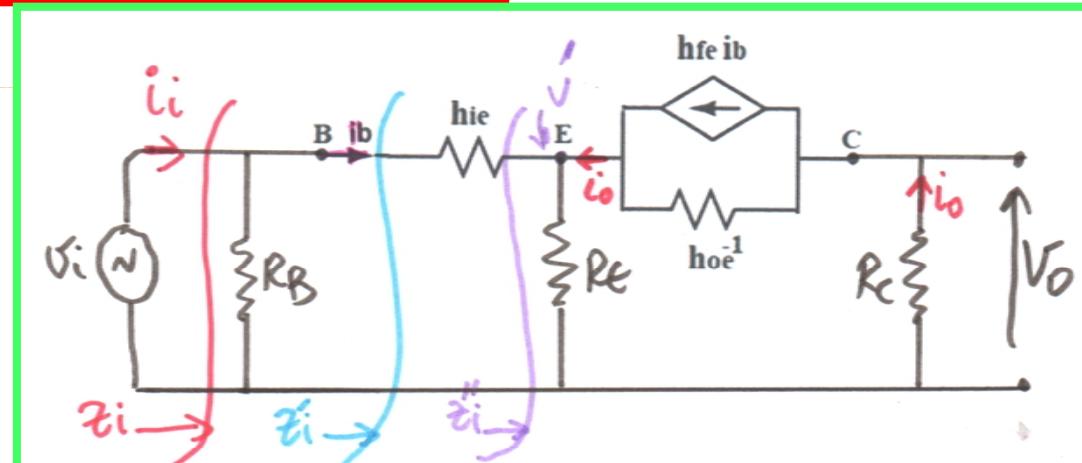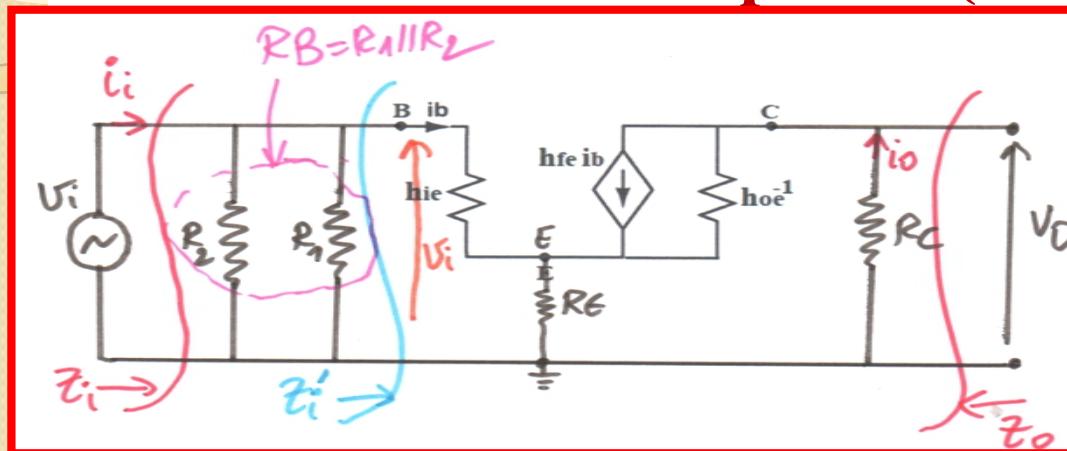


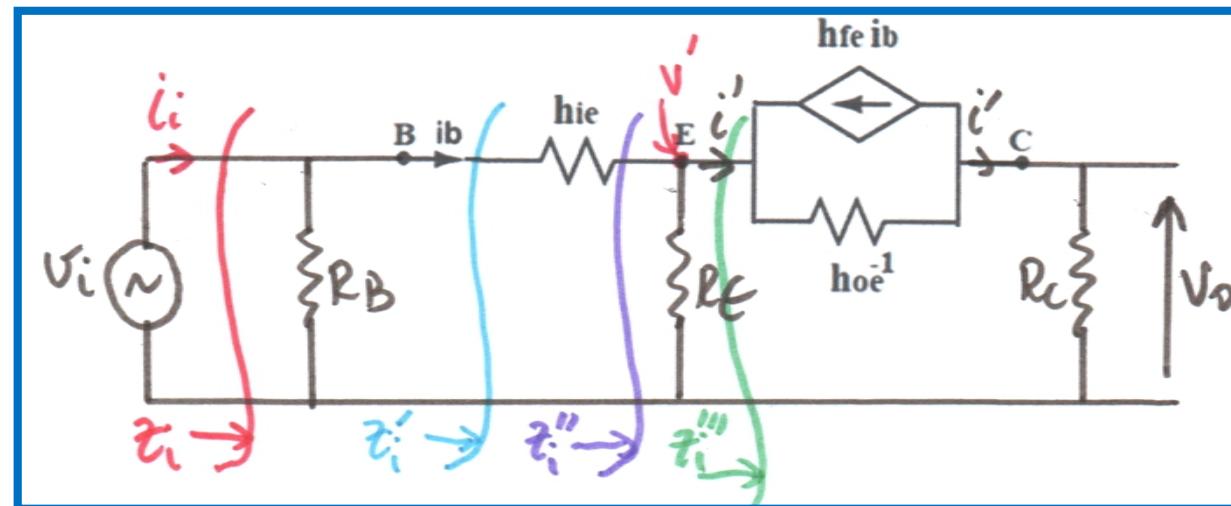App 2: Common Emitter Voltage divider bias amplifier (unbypassed R_E)



$$z_i = \frac{V_i}{i_i}$$

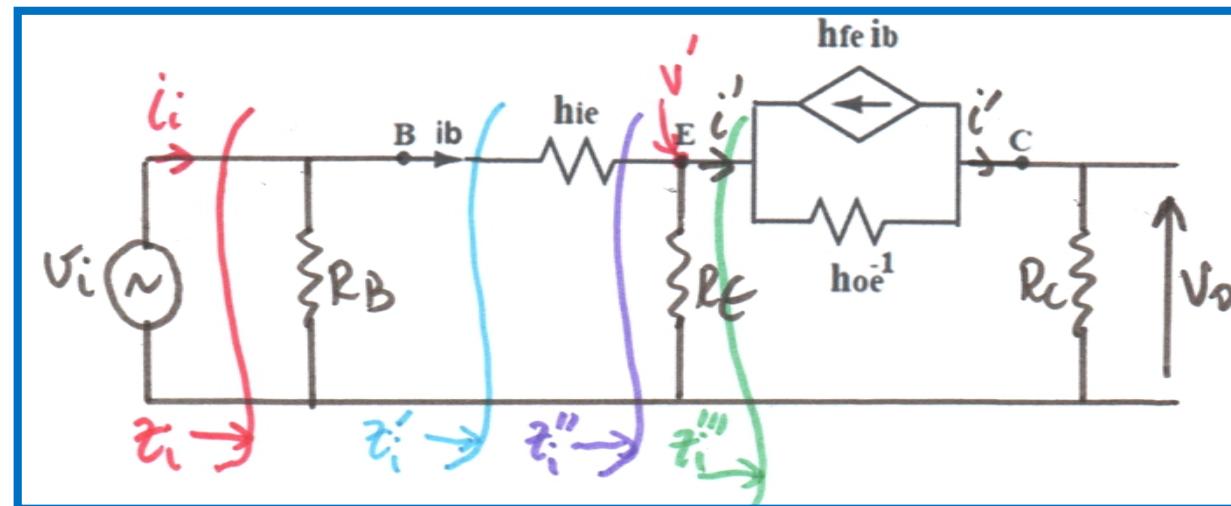
App 2: Common Emitter Voltage divider bias amplifier (unbypassed R_E)



$$Z_i = R_B \parallel Z_i'$$


$$Z_i' = \frac{V_i}{i_b}$$

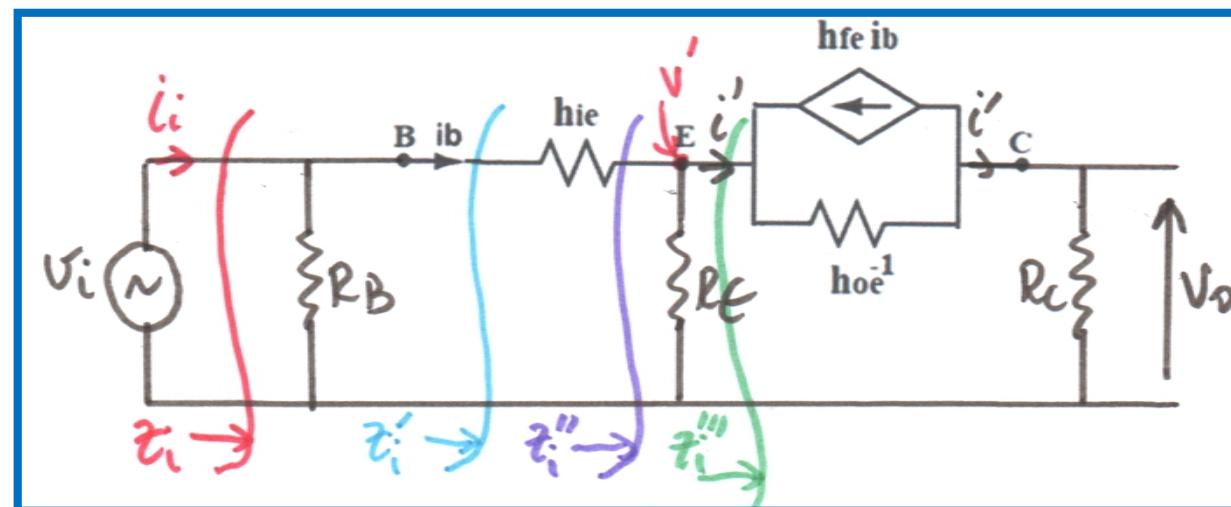App 2: Common Emitter Voltage divider bias amplifier (unbypassed R_E)




$$Z_i = R_B \parallel [h_{ie} + Z_{i''}]$$

$$Z_{i''} = \frac{V'}{i_b}$$

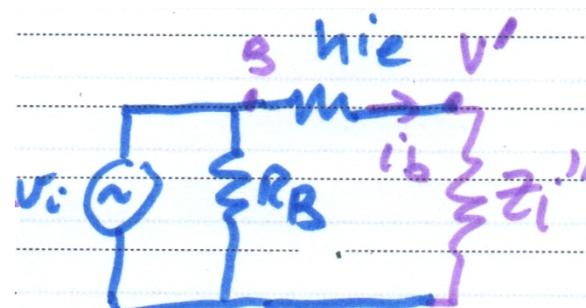


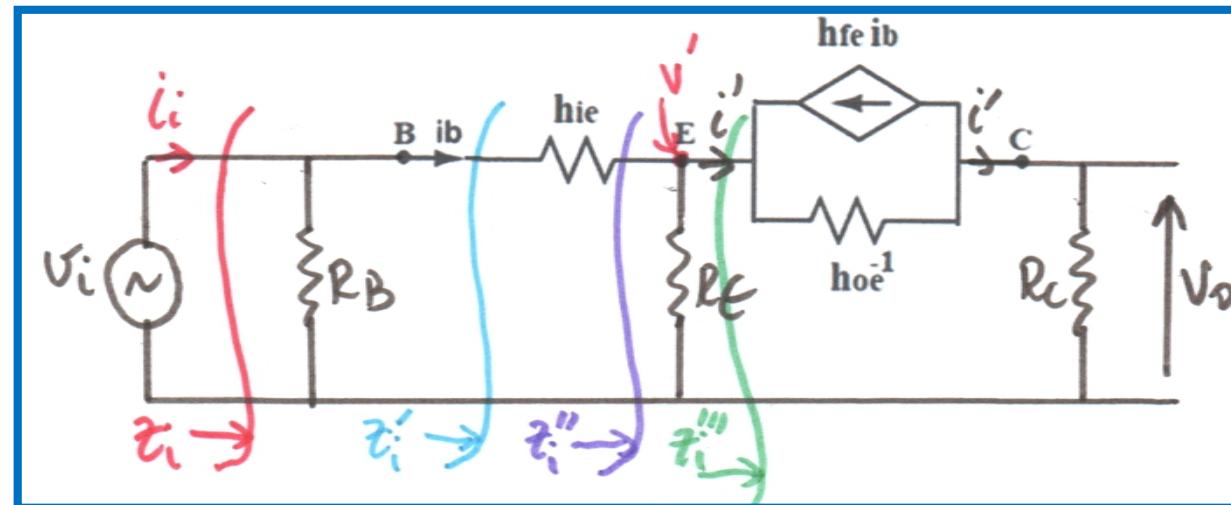App 2: Common Emitter Voltage divider bias amplifier (unbypassed R_E)




$$z_i = R_B \parallel [h_{ie} + (R_E \parallel z_i'')]$$

$$z_i''' = \frac{V'}{I'}$$

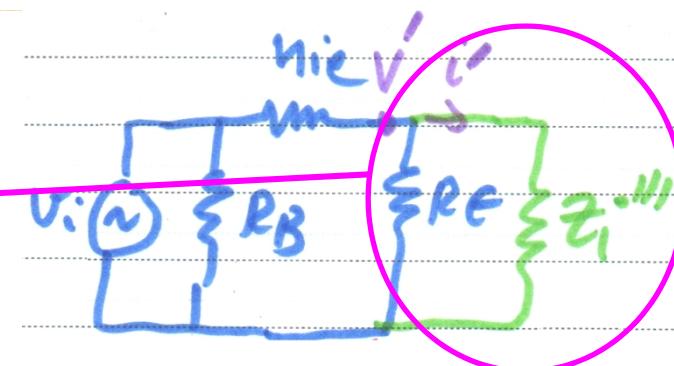

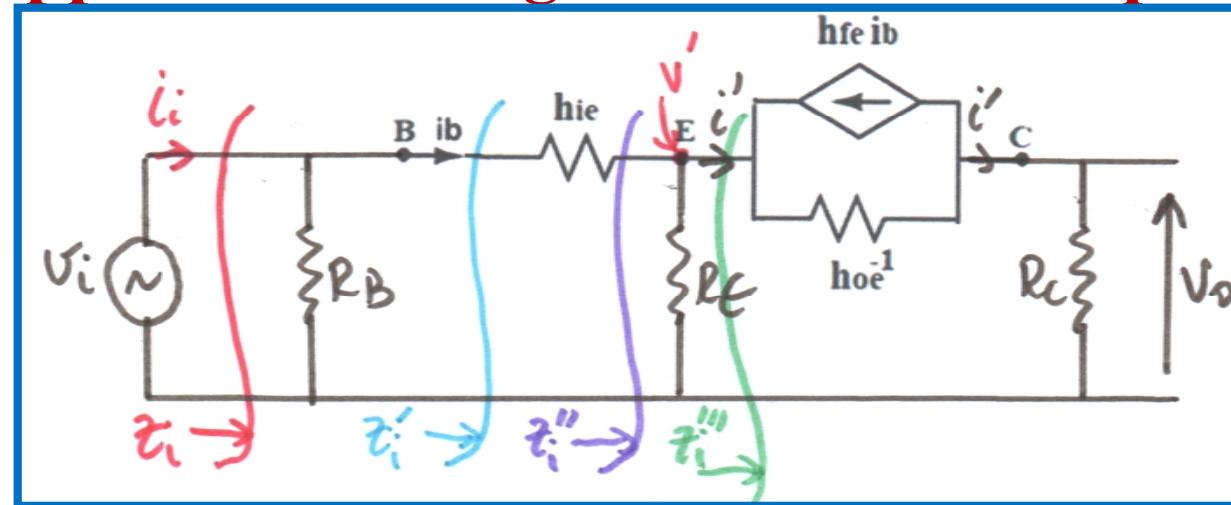App 2: C-E Voltage divider bias amplifier



$$z'_i = R_B / |z'_i|$$

$$z'_i = \frac{V_i}{i_b}$$

$$V_i = h_{ie} i_b + h_{oe}^{-1} (i'_c + h_{fe} i_b) + R_C i'_c \dots ①$$

$$V_i = h_{ie} i_b + R_E (i_b - i'_c) \dots ②$$

$$\textcircled{2} \Rightarrow i'_c = \frac{(h_{ie} + R_E) i_b - V_i}{R_E} \dots ③$$

App 2: C-E Voltage divider bias amplifier


③ in ①

$$V_i \left[1 + \frac{h_{oe}^{-1} + R_C}{R_E} \right] = i_b \left[h_{ie} + h_{oe}^{-1} h_{fe} + (h_{oe}^{-1} + R_C) \left(\frac{h_{ie} + R_E}{R_E} \right) \right]$$

$$Z'_i = \frac{V_i}{i_b} = \frac{h_{ie} + h_{oe}^{-1} h_{fe} + [(h_{oe}^{-1} + R_C)(h_{ie} + R_E)/R_E]}{1 + [(h_{oe}^{-1} + R_C)/R_E]}$$

$$Z_i = R_B // Z'_i$$

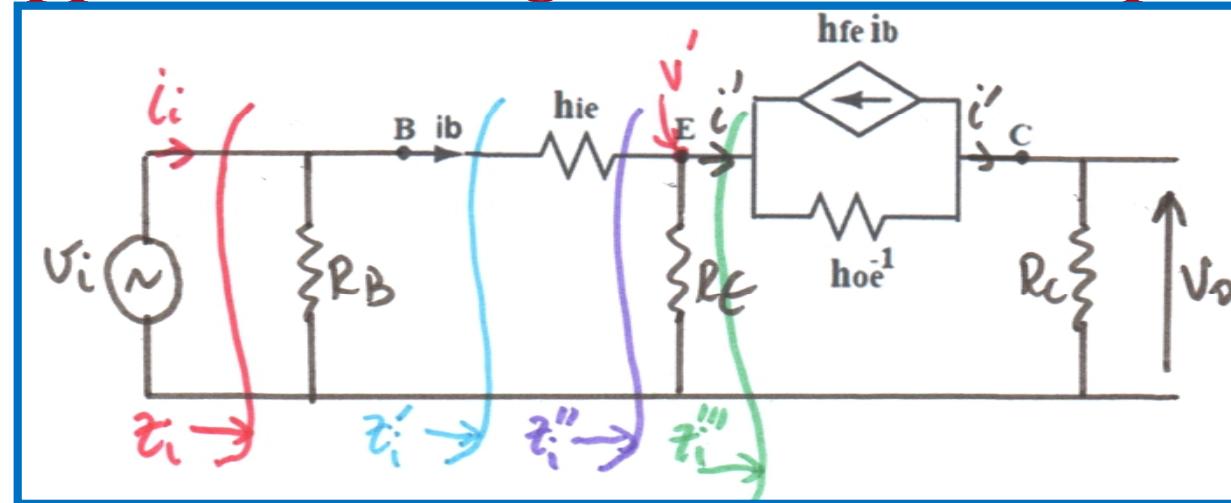App 2: C-E Voltage divider bias amplifier




$$A_v = \frac{V_o}{V_i}$$

$$V_i = h_{ie} i_b + h_{oe}^{-1} (i'_c + h_{fe} i_b) + V_o \dots \textcircled{1}$$

$$V_i = (h_{ie} + h_{oe}^{-1} h_{fe}) i_b + h_{oe}^{-1} i'_c + V_o \dots \textcircled{1}'$$

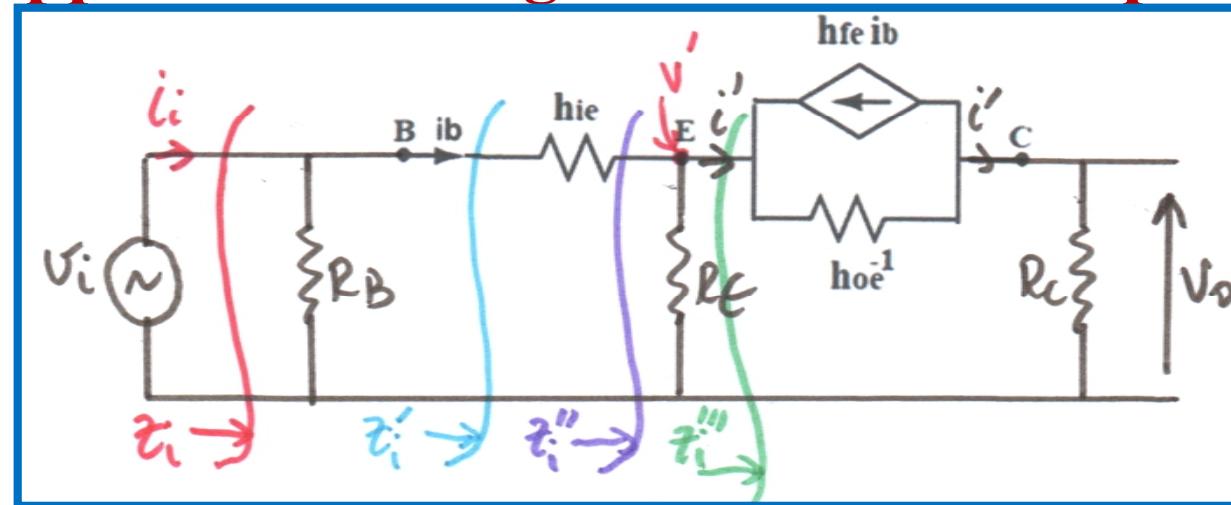
App 2: C-E Voltage divider bias amplifier



$$i_c' = \frac{V_o}{R_C} \dots \textcircled{2}$$

$$i_b = \frac{V_i}{z_i'} \dots \textcircled{3}$$

$\textcircled{2}$ and $\textcircled{3}$ in $\textcircled{1}$

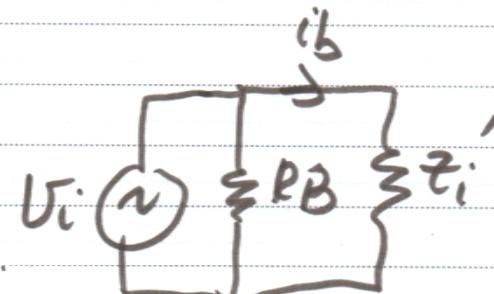

App 2: C-E Voltage divider bias amplifier


② and ③ in ①'

$$V_i = (h_{ie} + h_{oe}^{-1} h_{fe}) \frac{V_i}{Z_i'} + h_{oe}^{-1} \frac{V_o}{R_C} + V_o$$


$$V_i \left[1 - \frac{h_{ie} + h_{oe}^{-1} h_{fe}}{Z_i'} \right] = V_o \left[1 + \frac{h_{oe}^{-1}}{R_C} \right]$$

$$AV = \frac{V_o}{V_i} = \frac{1 - (h_{ie} + h_{oe}^{-1} h_{fe}) / Z_i'}{1 + \frac{h_{oe}^{-1}}{R_C}}$$

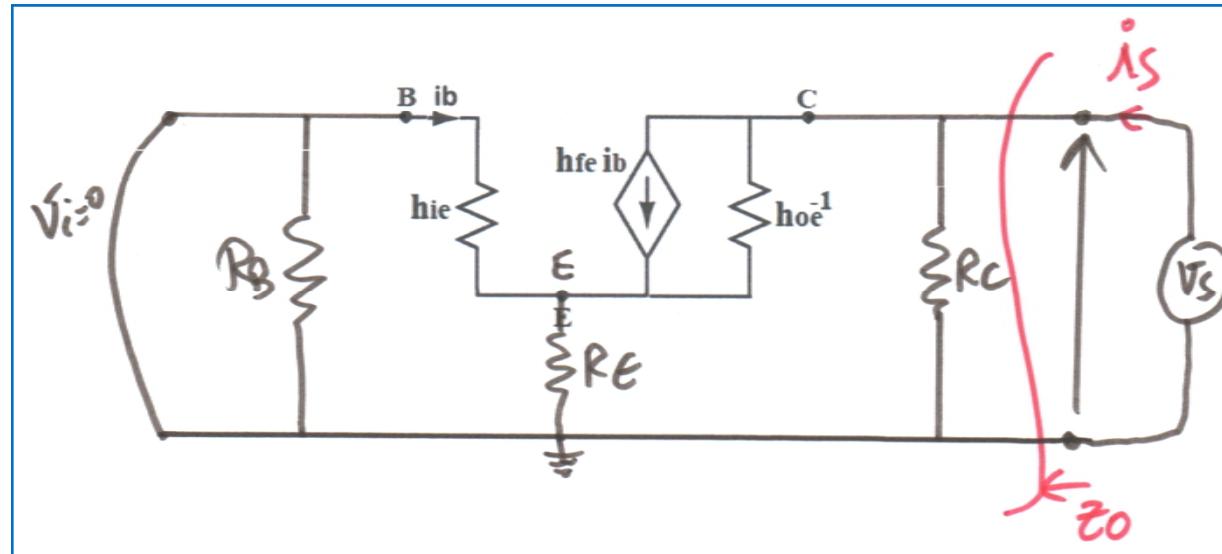App 2: C-E Voltage divider bias amplifier



$$Z_o = \frac{V_o}{i_s} |_{V_i=0}$$


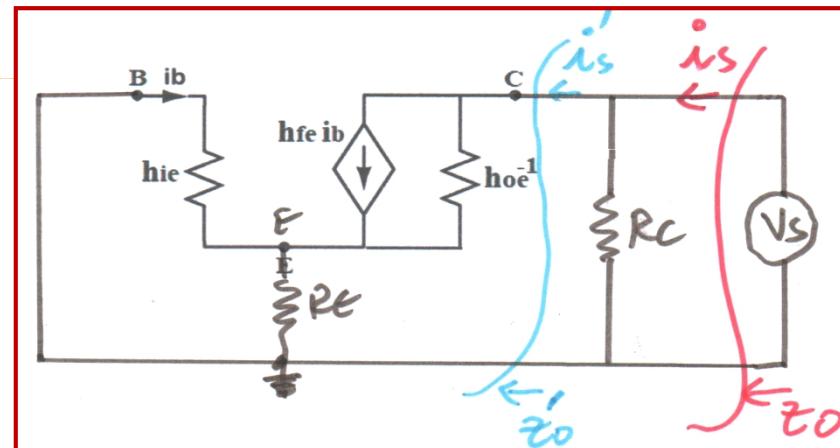


App 2: C-E Voltage divider bias amplifier


$$Z_0 = \frac{V_S}{i_s} |_{i_O=0}$$

$$Z_0 = R_C \| \frac{V_S}{i_s'} Z_0'$$

$$Z_0' = \frac{V_S}{i_s'}$$

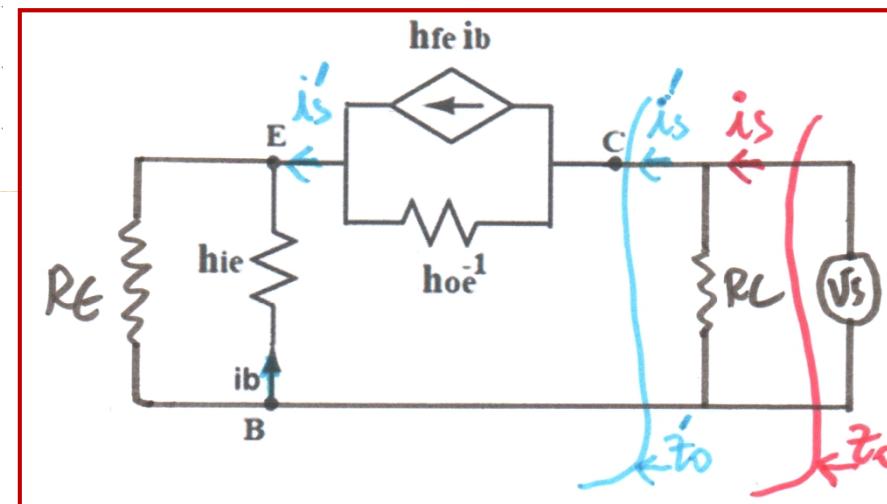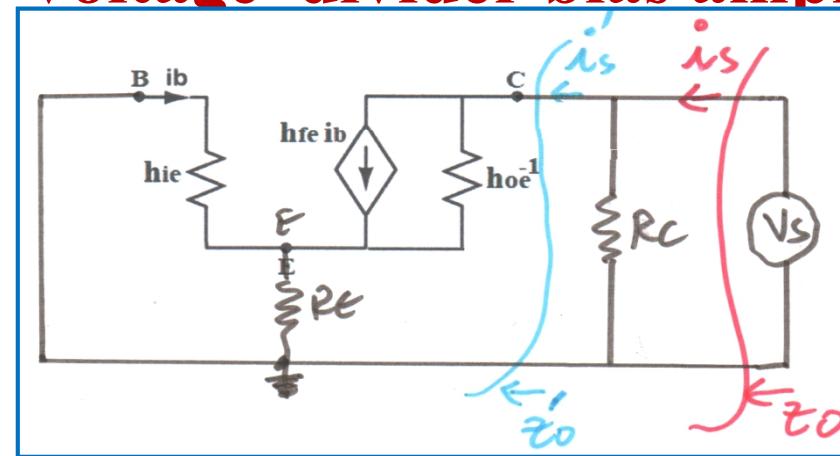

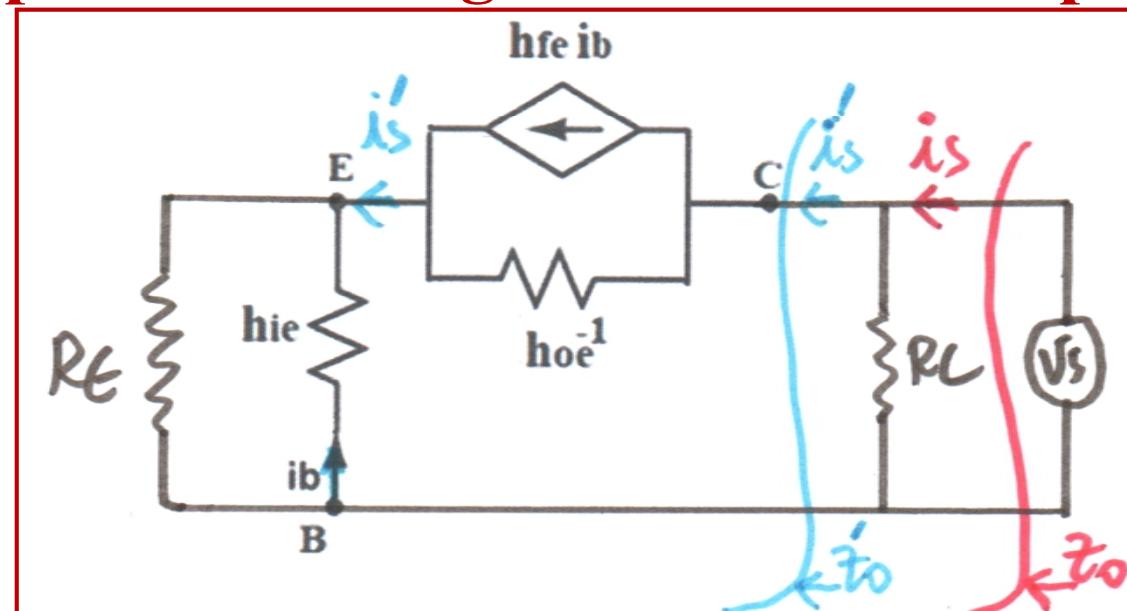
App 2: C-E Voltage divider bias amplifier



$$V_S = h_{oe}^{-1}(i_s' - h_{fe}i_b) + (h_{ie}/R_E)i_s' \dots \textcircled{1}$$

$$i_b = -\frac{R_E}{R_E + h_{ie}} i_s' \dots \textcircled{2}$$

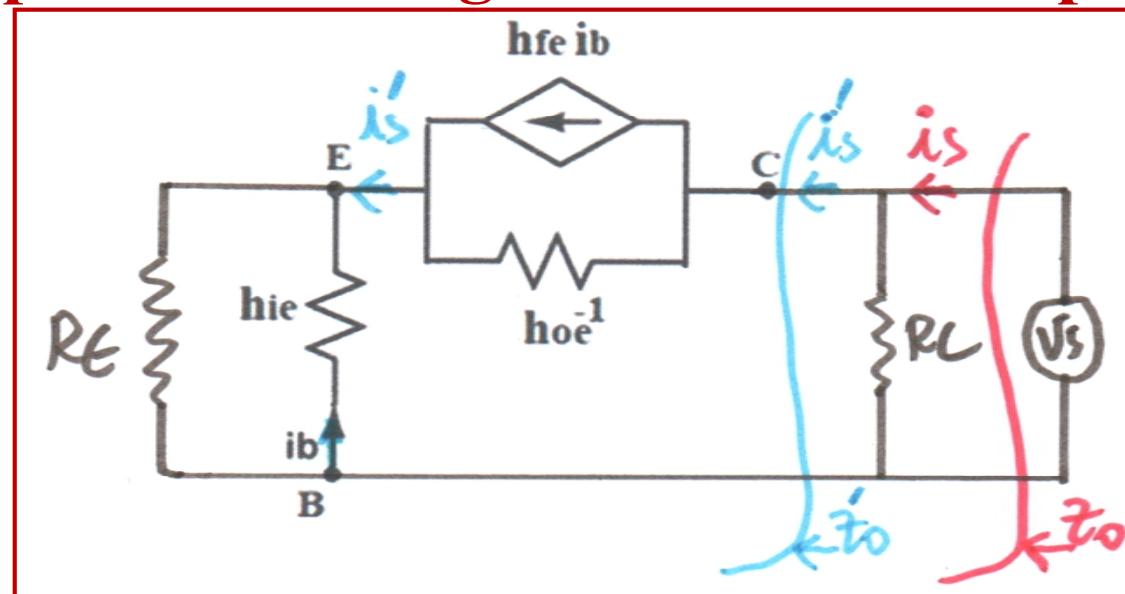
App 2: C-E Voltage divider bias amplifier



$$V_S = h_{oe}^{-1}(i_S - h_{fe}i_b) + (h_{ie}/R_E)i_S \dots \textcircled{1}$$

$$i_b = -\frac{R_E}{R_E + h_{ie}} i_S \dots \textcircled{2}$$

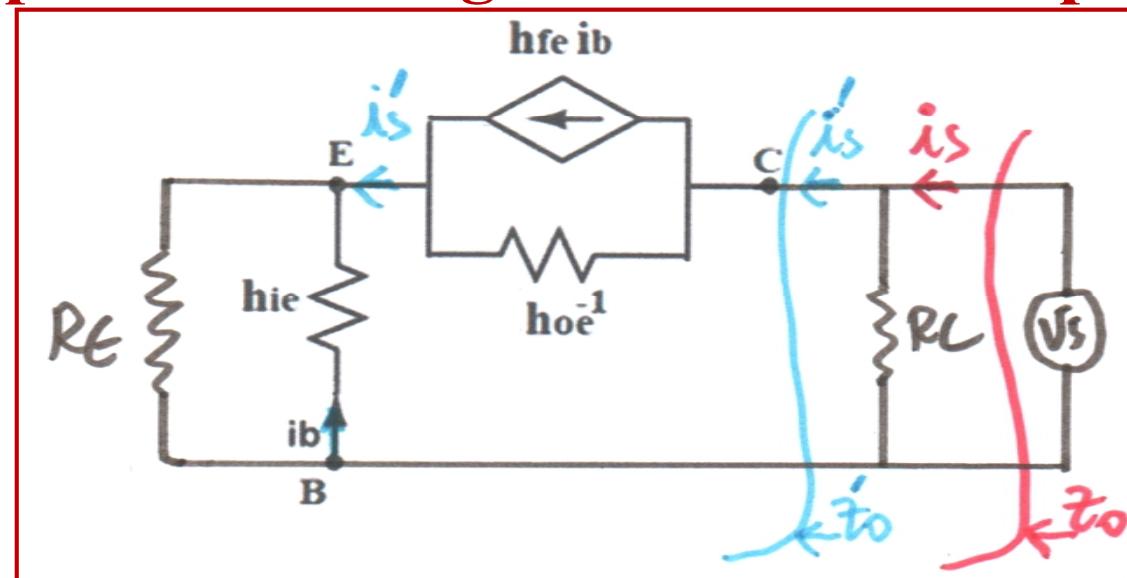App 2: C-E Voltage divider bias amplifier




② in ①

$$Z_0' = \frac{V_S}{I_{S'}} = h_{oe}^{-1} + (h_{ie} \| R_E) + \frac{h_{oe}^{-1} h_{fe} R_E}{R_E + h_{ie}}$$

$$Z_0 = R_C \| Z_0'$$

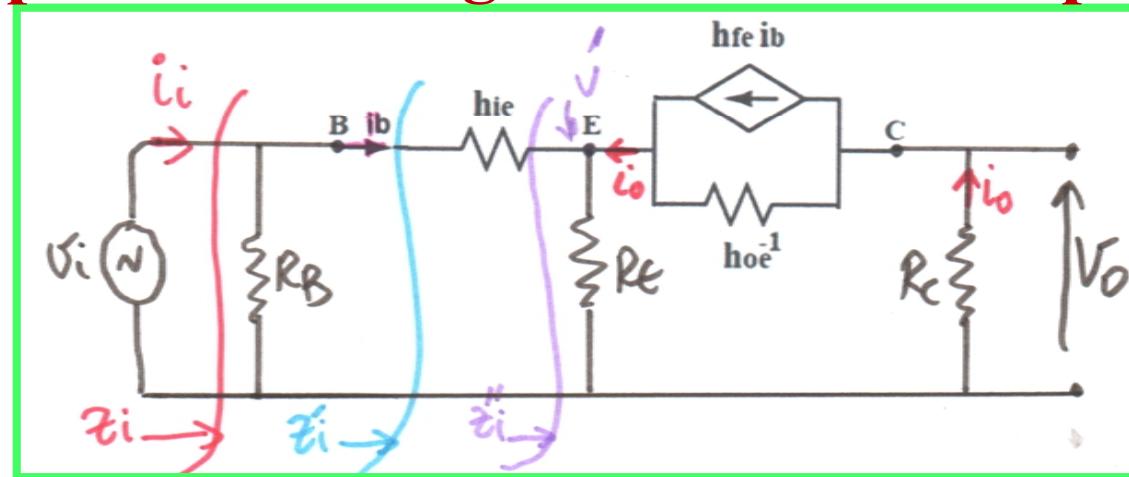App 2: C-E Voltage divider bias amplifier



$$A_i = \frac{i_o}{i_i}$$

$$V_i = z_i i_i \quad \text{--- (1)}$$

$$V_o = -R_C i_o \quad \text{--- (2)}$$

$$\Rightarrow \frac{V_o}{V_i} = -\frac{R_C}{z_i} \frac{i_o}{i_i}$$

$$\boxed{A_i = -\frac{z_i}{R_C} A_V}$$

App 2: C-E Voltage divider bias amplifier

Config.	C-E (bypass. R_E)	C-E (unbypass. R_E)	C-B	C-C
Z_i	Medium	High	Low	High
Z_o	M	M	M	L
A_{VNL}	H (<0)	M(<0)	H(>0)	L($\approx I$)
A_i	H (>0)	H(>0)	L($\approx -I$)	H (<0)

hie??

$$hie = \frac{\Delta V_{BE}}{\Delta I_B} |_{I_B}$$

$$I_B = I_s e^{\frac{V_{BE}}{V_T}}$$

$$\frac{\partial I_B}{\partial V_{BE}} = I_s e^{\frac{V_{BE}}{V_T}} \frac{1}{V_T} I_B$$

↓

$$hie = \frac{\partial V_{BE}}{\partial I_B} = \frac{V_T}{I_B}$$

$$I_B = \beta$$

$$I_B = \frac{I_C}{\beta} \approx \frac{I_C}{hie}$$

$$hie = h_f e \frac{V_T}{I_C}$$

V_T: Thermal Voltage

End of presentation