

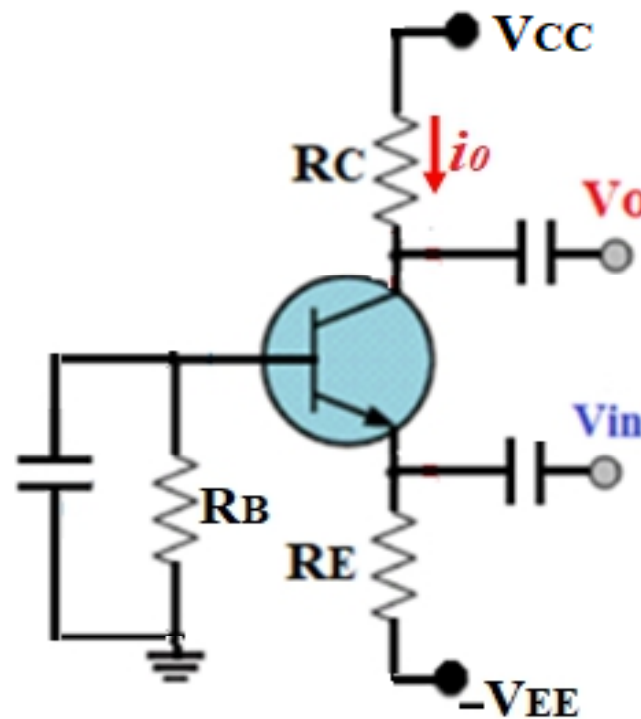




App 3: Common Base configuration

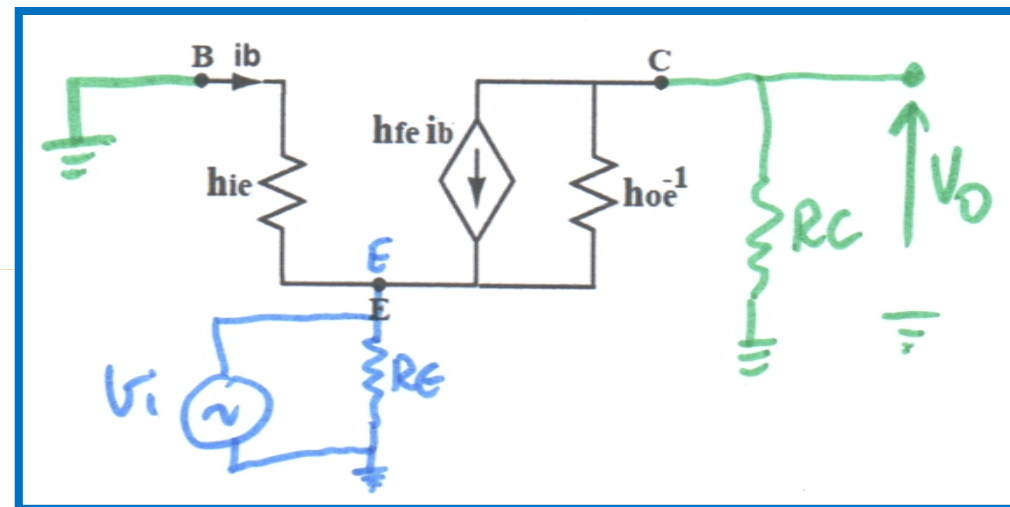


App 3: Common Base configuration

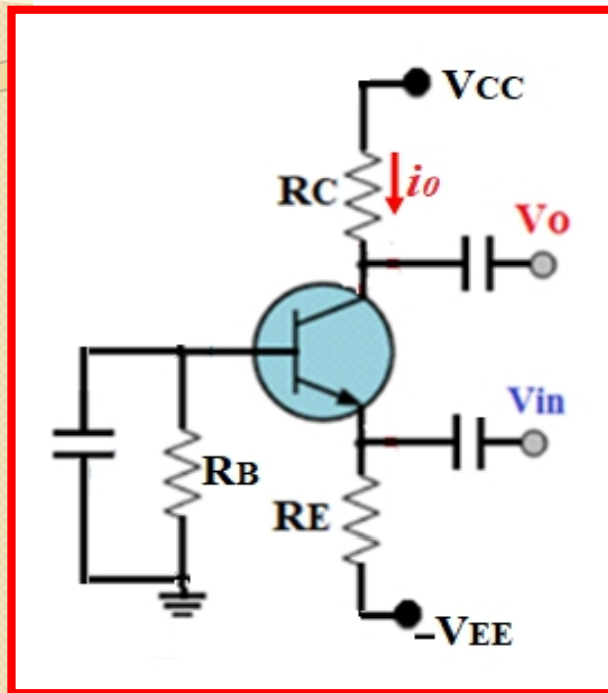

App 3: Common Base configuration

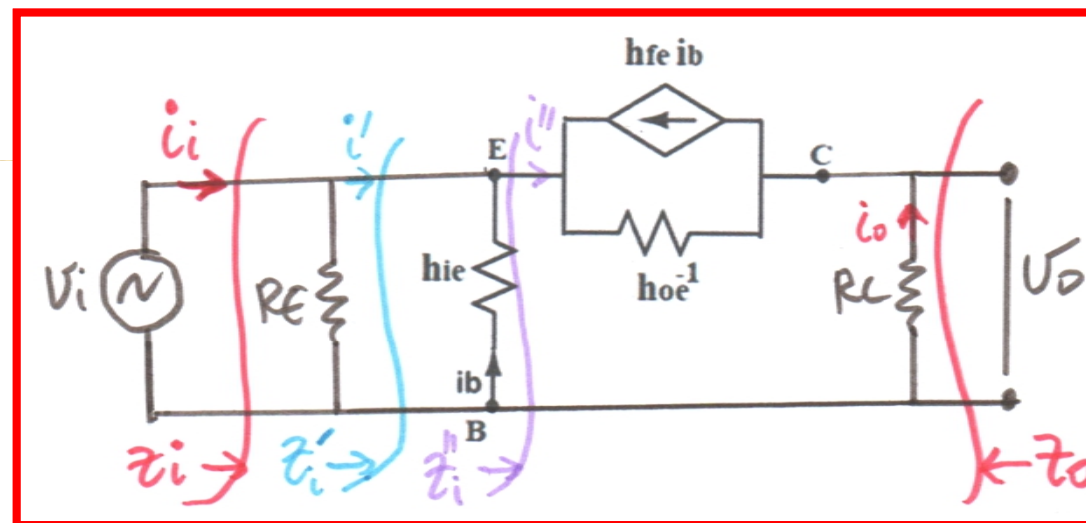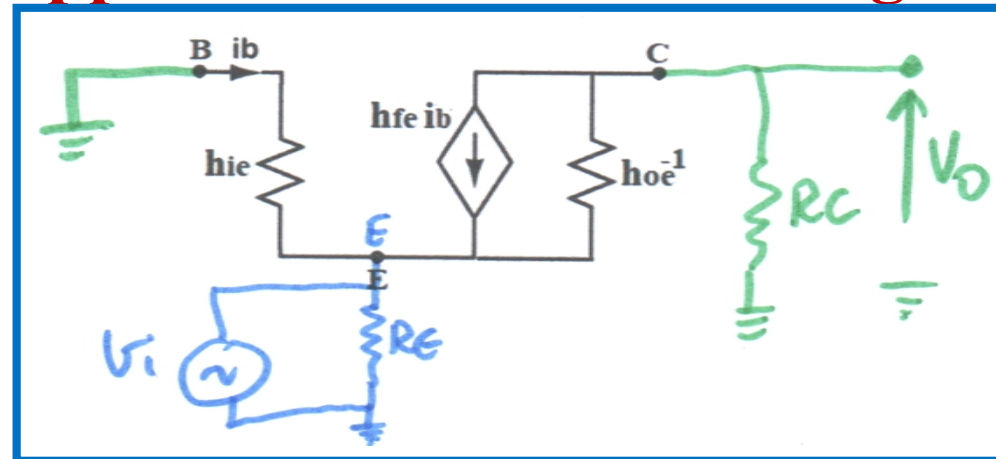

App 3: Common Base configuration

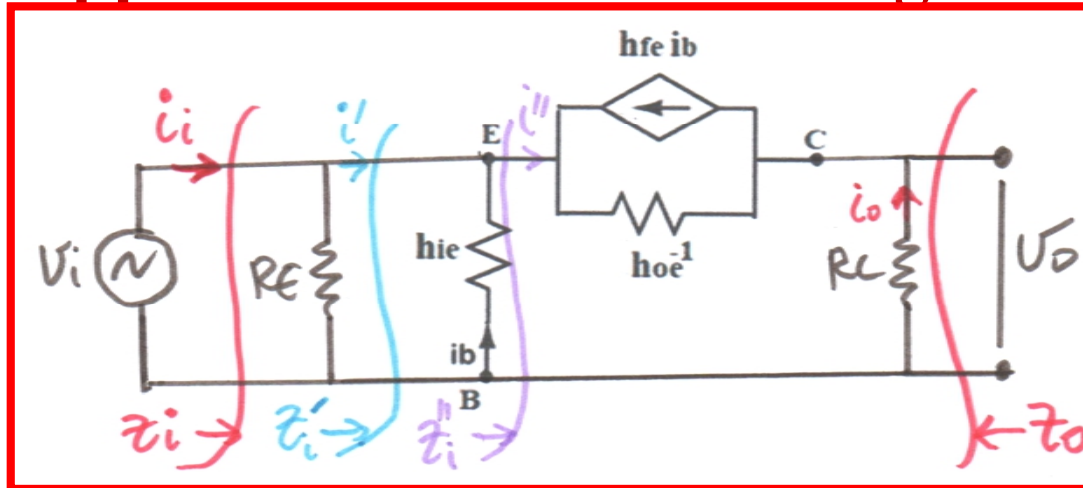

$$z_i = \frac{V_i}{i_i} ?$$


$$z_i = R_E \parallel h_{ie} \parallel z_i''$$

$$z_i'' = \frac{V_i}{i''}$$

$$V_i = h_{oe}^{-1} (i'' + h_{fe} i_b) + R_C i''$$

$$V_i = (h_{oe}^{-1} + R_C) i'' + h_{oe}^{-1} h_{fe} i_b \dots \textcircled{1}$$

App 3: Common Base configuration

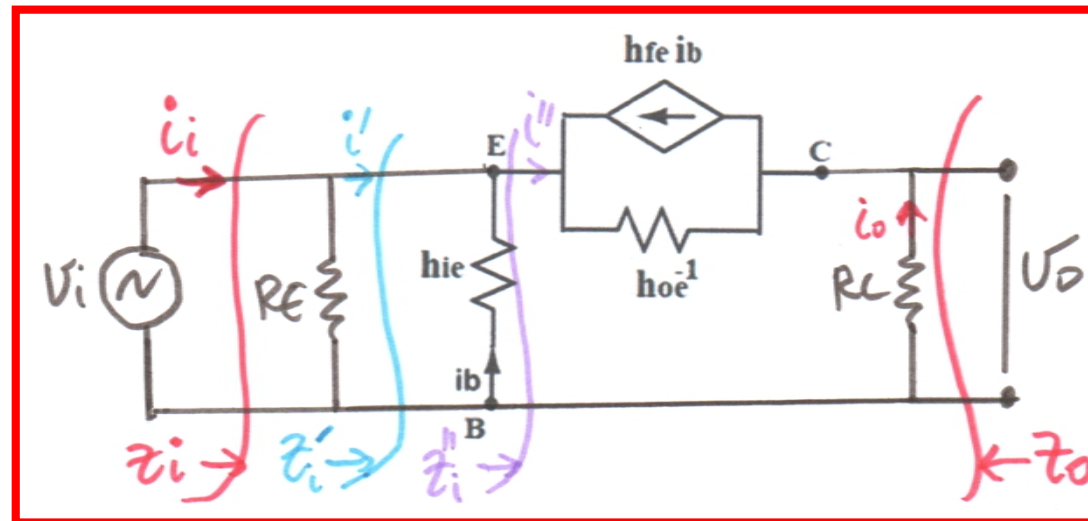


$i_b?$

$$V_i = -h_{ie} i_b \Rightarrow i_b = -\frac{V_i}{h_{ie}} \dots (2)$$

(2) in (1):


App 3: Common Base configuration

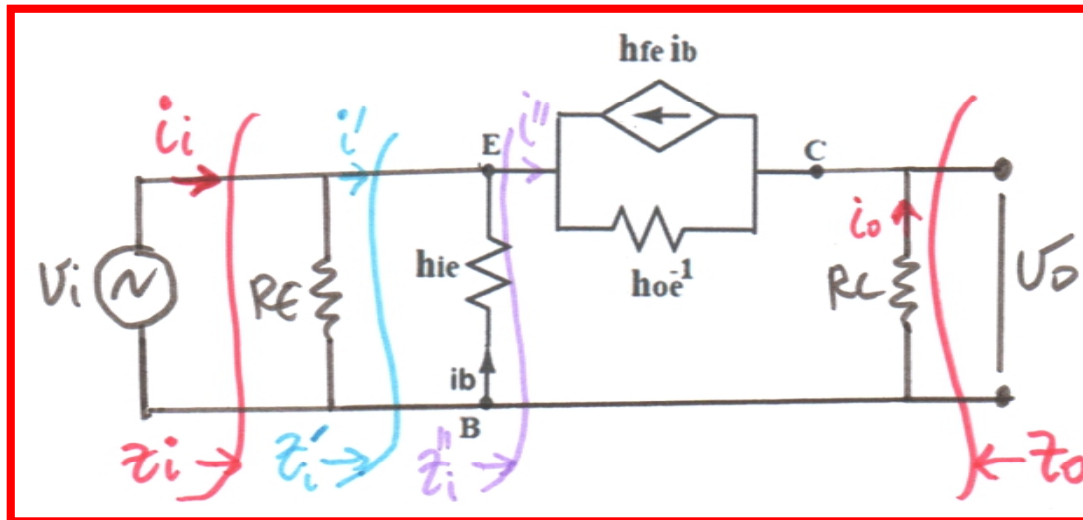

$$V_i \left[1 + \frac{h_{oe}^{-1} h_{fe}}{h_{ie}} \right] = (h_{oe}^{-1} + R_C) i''$$

$$z_i'' = \frac{V_i}{i''} = \frac{h_{oe}^{-1} + R_C}{1 + \frac{h_{oe}^{-1} h_{fe}}{h_{ie}}}$$

App 3: Common Base configuration

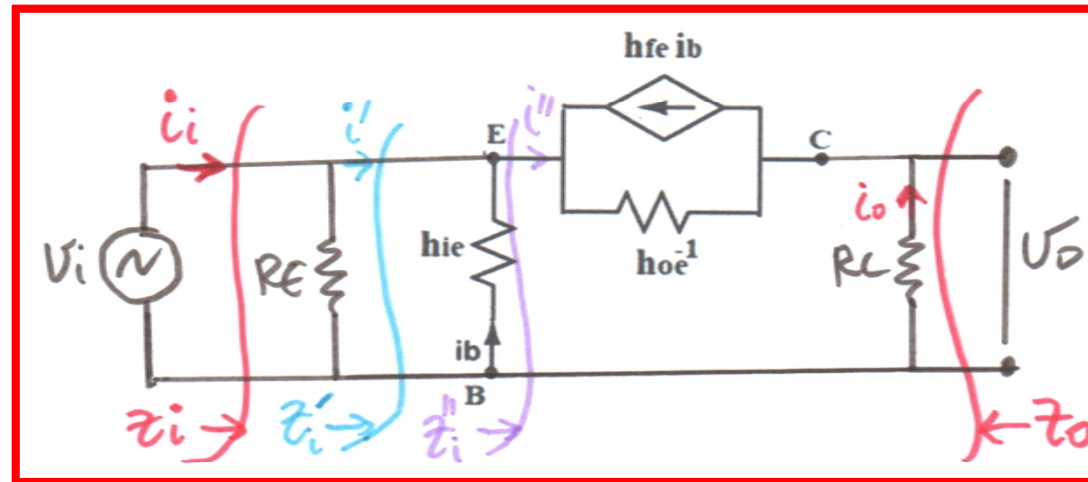

$$z_i'' = \frac{V_i}{i''} = \frac{h_{oe} + R_C}{1 + \frac{h_{oe} h_{fe}}{h_{ie}}}$$



If $h_{oe}^{-1} = \infty$

$$z_i'' = \frac{h_{ie}}{h_{fe}} \ll$$

$$z_i = R_E \parallel h_{ie} \parallel z_i''$$

$$z_i = R_E \parallel h_{ie} \parallel z_i'' \ll$$

App 3: Common Base configuration

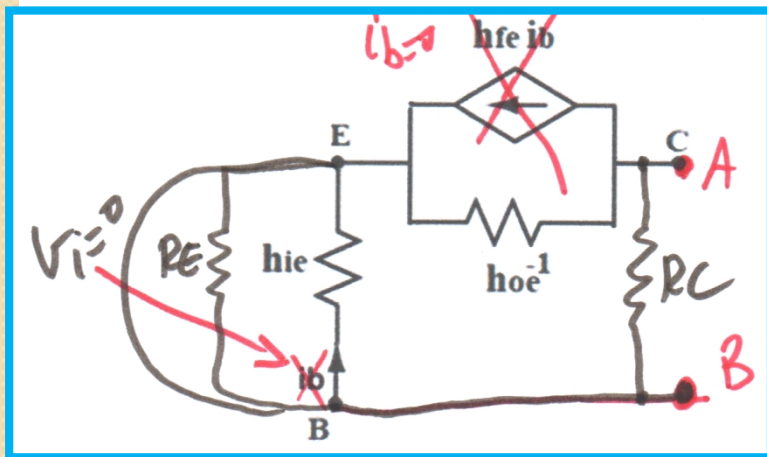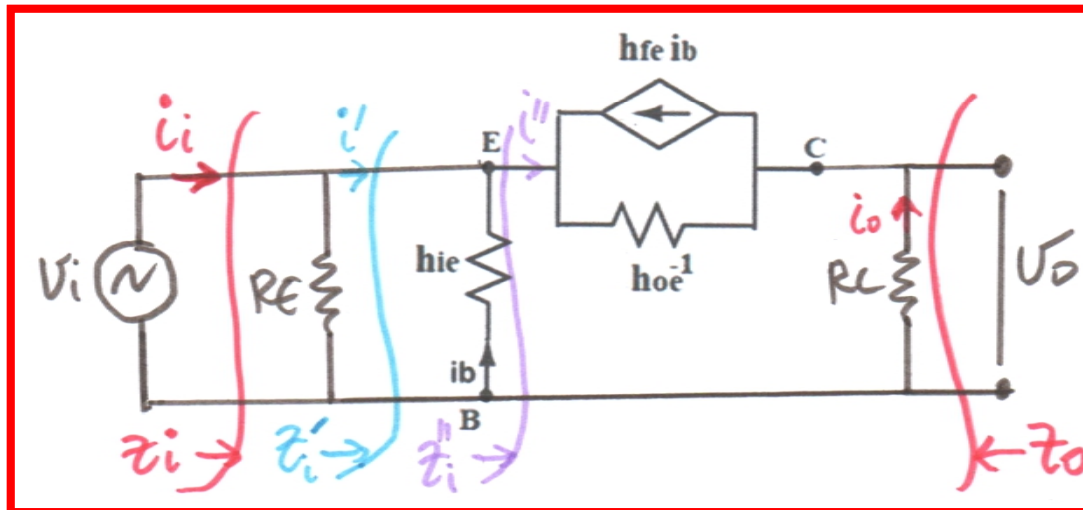


$z_o / V_i = 0$??

$$z_o = h_{oe}^{-1} \parallel R_C$$

z_o : Medium

App 3: Common Base configuration

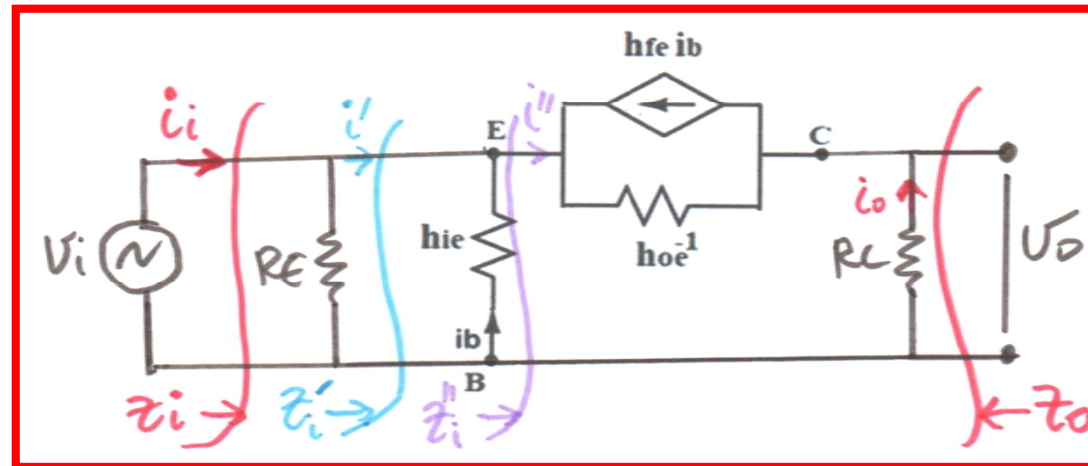

$$A_{V_{NL}} = \frac{V_o}{V_i} ?$$


$$V_i = h_{oe}^{-1}(i'' + h_{fe}i_b) + V_o \dots (1)$$

$$i'' = \frac{V_o}{R_C} \dots (2) \quad i_b = -\frac{V_i}{h_{ie}} \dots (3)$$

(2) and (3) in (1)

$$A_{V_{NL}} = \frac{V_o}{V_i} = \frac{1 + \frac{h_{fe} h_{oe}^{-1}}{h_{ie}}}{1 + \frac{h_{oe}^{-1}}{R_C}}$$


App 3: Common Base configuration

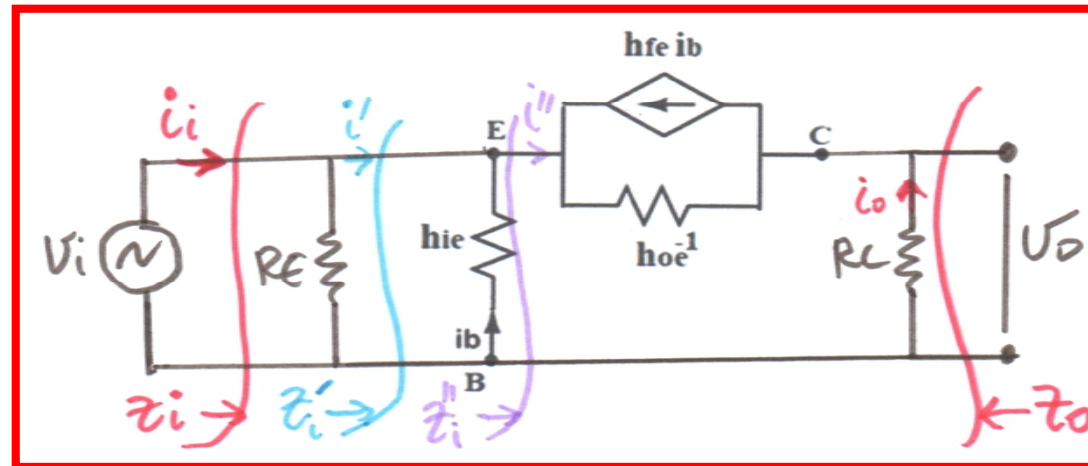

$$A_{V_{NL}} = \frac{V_o}{V_i} = \frac{1 + \frac{h_{fe} h_{oe}^{-1}}{h_{ie}}}{1 + \frac{h_{oe}^{-1}}{R_C}}$$

$$\left. \begin{aligned} h_{oe}^{-1} &= \infty \\ A_{V_{NL}} &= \frac{R_C h_{fe}}{h_{ie}} \end{aligned} \right\} A_{V_{NL}} \uparrow$$

App 3: Common Base configuration

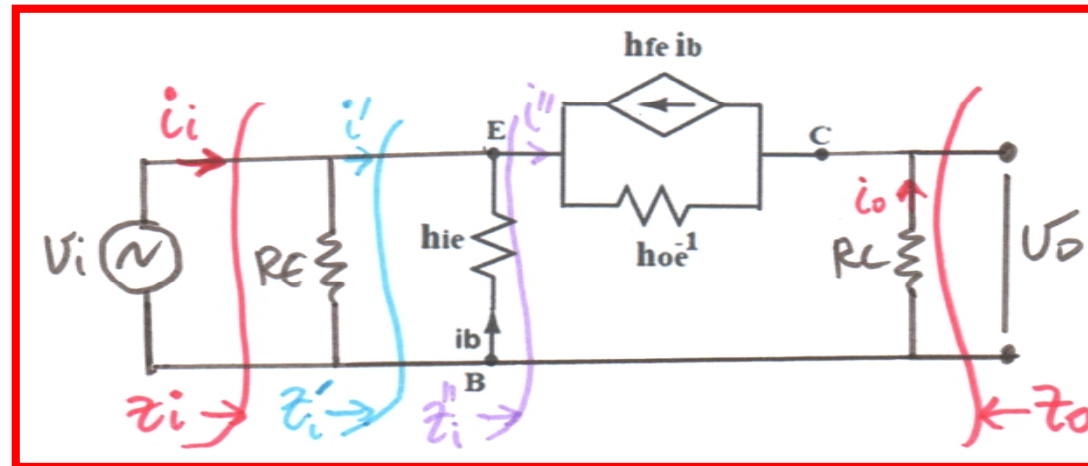

$$A_i = -\frac{z_i}{R_C} A_{V_{NL}}$$

$$A_i < 0 \text{ and } |A_i| < 1$$

App 3: Common Base configuration

Config.	C-E (bypass. R_E)	C-E (unbypass. R_E)	C-B	C-C
Z_i	Medium	High	Low	High
Z_o	M	M	M	L
AV_{NL}	H (<0)	M(<0)	H(>0)	L(≈ 1)
A_i	H (>0)	H(>0)	L(≈ -1)	H (<0)

End of presentation